

# SERIES VS. PARALLEL COMPARISON SHEET

SERIES	PARALLEL
<p><u>CURRENT OR AMPERES</u></p> <p>A. 1 PATH TO FOLLOW</p> <p>B. ALWAYS THE SAME EVERYWHERE</p> <p>C. <math>I_{TOTAL} = I_1 = I_2 = I_3 = \dots\dots</math></p> <p>D. <math>I = E/R</math></p>	<p><u>CURRENT OR AMPERES</u></p> <p>A. MORE THAN 1 PATH</p> <p>B. THE SUM OF ALL BRANCH CURRENTS</p> <p>C. <math>I_{TOTAL} = I_1 + I_2 + I_3 + \dots\dots</math></p> <p>D. <math>I = E/R</math></p>
<p><u>EMF OR VOLTAGE</u></p> <p>A. TOTAL VOLTS = SUM OF ALL RESISTOR VOLTS</p> <p><math>V_{TOTAL} = V_1 + V_2 + V_3 + \dots\dots</math>  <math>(E_{TOTAL} = E_1 + E_2 + E_3 + \dots\dots)</math></p> <p>B. <math>E = IR</math></p>	<p><u>EMF OR VOLTAGE</u></p> <p>A. ALL RESISTANCES (LOADS) GET FULL EMF OR VOLTAGE</p> <p><math>V_{TOTAL} = V_1 = V_2 = V_3 = \dots\dots</math>  <math>(E_{TOTAL} = E_1 = E_2 = E_3 = \dots\dots)</math></p> <p>B. <math>E = IR</math></p>
<p><u>RESISTANCE (OHMS)</u></p> <p>A. TOTAL RESISTANCE IS THE SUM OF ALL THE RESISTORS</p> <p><math>R_{TOTAL} = R_1 + R_2 + R_3 + \dots\dots</math></p> <p>B. <math>R = E/I</math></p> <p>C. AS YOU ADD RESISTORS IN SERIES:</p> <p>RESISTANCE GOES UP</p> <p>CURRENT GOES DOWN</p>	<p><u>RESISTANCE (OHMS)</u></p> <p>A. TOTAL RESISTANCE IS THE SUM OF THE RECIPROCAL</p> <p><math>1/R_{TOTAL} = 1/R_1 + 1/R_2 + 1/R_3</math>  <small>(then invert answer or take reciprocal)</small></p> <p>B. <math>R = E/I</math></p> <p>C. AS YOU ADD RESISTORS IN PARALLEL:</p> <p>RESISTANCE GOES DOWN</p> <p>CURRENT GOES UP</p>